

# Linear Feedback Shift Register (LFSR)


## Definition

An LFSR is a shift register where the input bit is determined by a linear function of its current state. In digital logic (GF(2)), this linear function is strictly XOR.
 
## Structure and Operation

The LFSR shifts bits at every clock cycle. The new bit entering the register is calculated by XORing specific bits currently in the register.

- **Taps:**  
These are the specific bit positions that are XORed together to determine the next state.
- **Polynomial Representation:**



The tap configuration is often expressed as a "characteristic polynomial." For example, a 16-bit LFSR using taps at positions 16, 14, 13, and 11 is written as:

$$S(x) = x^{16} + x^{14} + x^{13} + x^{11} + 1$$

The exponents correspond to the tap positions.

- **Seed:**  
This is the initial value loaded into the register. The LFSR must be initialized with a non-zero seed to operate (In XOR logic).

## Properties

When designed with a "primitive polynomial," an LFSR exhibits properties ideal for pseudo-random number generation (PRNG):

- **Maximum Length Period:**  
For an  $n$ -bit register, the sequence will repeat only after  $2^n - 1$  cycles. It cycles through every possible state except the all-zero state (which would cause a lock-up).
- **Deterministic:**  
While the output looks random, the sequence is deterministic. If you know the current state and the polynomial, you can predict the next bit.
- **Distribution Balance:**  
The output stream is nearly unbiased (50% probability). In a full period, there are exactly  $2^{n-1}$  ones and  $2^{n-1} - 1$  zeros.
- **Run-Length Properties:**  
The distribution of consecutive "runs" (consecutive 1s or 0s) follows a specific statistical pattern: 50% of runs are length 1, 25% are length 2, 12.5% are length 3, etc.

# Generate pseudo-random number

---

Since the LFSR natively outputs a 1-bit stream with a ~50% uniform distribution, we use specific digital logic structures to transform this into multi-bit values or weighted probabilities.

## 1. Generating Multi-bit Values (Bit-Width)

To generate an  $N$ -bit random integer (e.g., an 8-bit byte or 32-bit word), two primary methods are used:

- **Serial Accumulation (High Quality):**

Wait for  $N$  clock cycles, shifting the single output bit into a separate  $N$ -bit shift register.

- *Pros:* The bits in the generated word are mathematically uncorrelated.
- *Cons:* Throughput is lower (requires  $N$  cycles per word).

- **Parallel Slicing (High Speed):**

Take  $N$  bits directly from the LFSR's internal state in a single clock cycle.

- *Pros:* 1 word per clock cycle.
- *Cons:* Consecutive words are highly correlated (they are just shifted versions of the previous state).

## 2. Tunable Probability (Weighted Randomness)

To generate a random bit that is **logic '1' with probability  $P$**  (where  $P \neq 50\%$ ), we use the **Comparator Method**.

- **Structure:**

1. Generate an  $N$ -bit uniform random integer ( $R$ ) using the LFSR (as described above).
2. Define a Threshold ( $T$ ) such that  $T = P \times 2^N$ .
3. Compare:

$$Output = \begin{cases} 1 & \text{if } R < T \\ 0 & \text{if } R \geq T \end{cases}$$

- **Precision (Resolution):**

The "Probability Precision" is determined strictly by the **bit-width ( $N$ )** of the random integer used in the comparison.

- **Low Precision:** Using 8 bits ( $N = 8$ ) gives a resolution of  $1/256 \approx 0.39\%$ .
- **High Precision:** Using 32 bits ( $N = 32$ ) gives a resolution of  $1/2^{32} \approx 2.3 \times 10^{-10}$ .